

Zack Fravel

010646947

Lab 1 : M 4:10 - 5:55 PM

Lab 7 - Pipelined CPU

5/2/16

Introduction


The objectives of Lab 7 is to convert the Single-Cycle CPU we completed in lab 6 into a CPU that is implemented using pipelined instruction execution. What this allows us to do is get through our instructions much faster because we will have more than one instruction “in the pipeline” at any given time. This optimizes our CPU and allows us to execute more instructions in less time. However, it’s not all positive, with this pipelined design we also assume a few hazards, which we will have to take care of in our implementation.

Approach

The high level implementation of converting our Single-Cycle datapath into a Pipelined datapath is fairly simple. We want to break up our datapath into five phases: Instruction Fetch (IF), Instruction Decode (ID), Execute (EX), Memory (MEM), and Write-back (WB). Each one of these phases in our datapath is broken up by adding a simple generic-width register that was given to us in the lab description. This generic width allows us to set the width of the register in our system entity, since each of our buffers take in different amounts of data.

One thing we need to take into account when dealing with a pipelined datapath is different kinds of hazards. There are three different types of hazards: structural, data, and control hazards. In our lab, we have a few data and control hazards we need to take care of. First of all, because of the way our pipeline is set up, it is possible for the write-back address that we give to the register to complete an operation to change as another instruction moves along the pipeline, causing us to write to the wrong registers. Another thing that can happen is a branch cannot properly execute because we have the next 3 instructions after it already in the pipeline. What we need to do to take care of some of these hazards is add 3 nop instructions (x”0000”) after the

instructions where we have these issues. The way you figure this out is by looking where we have RAW (read-after-write) hazards, which would be an instruction using the destination register as an operand or a comparator immediately following the computation of that register. This is why we need to add nops, because we have actual hardware buffers between instructions. Below is a diagram of the datapath we are implementing.

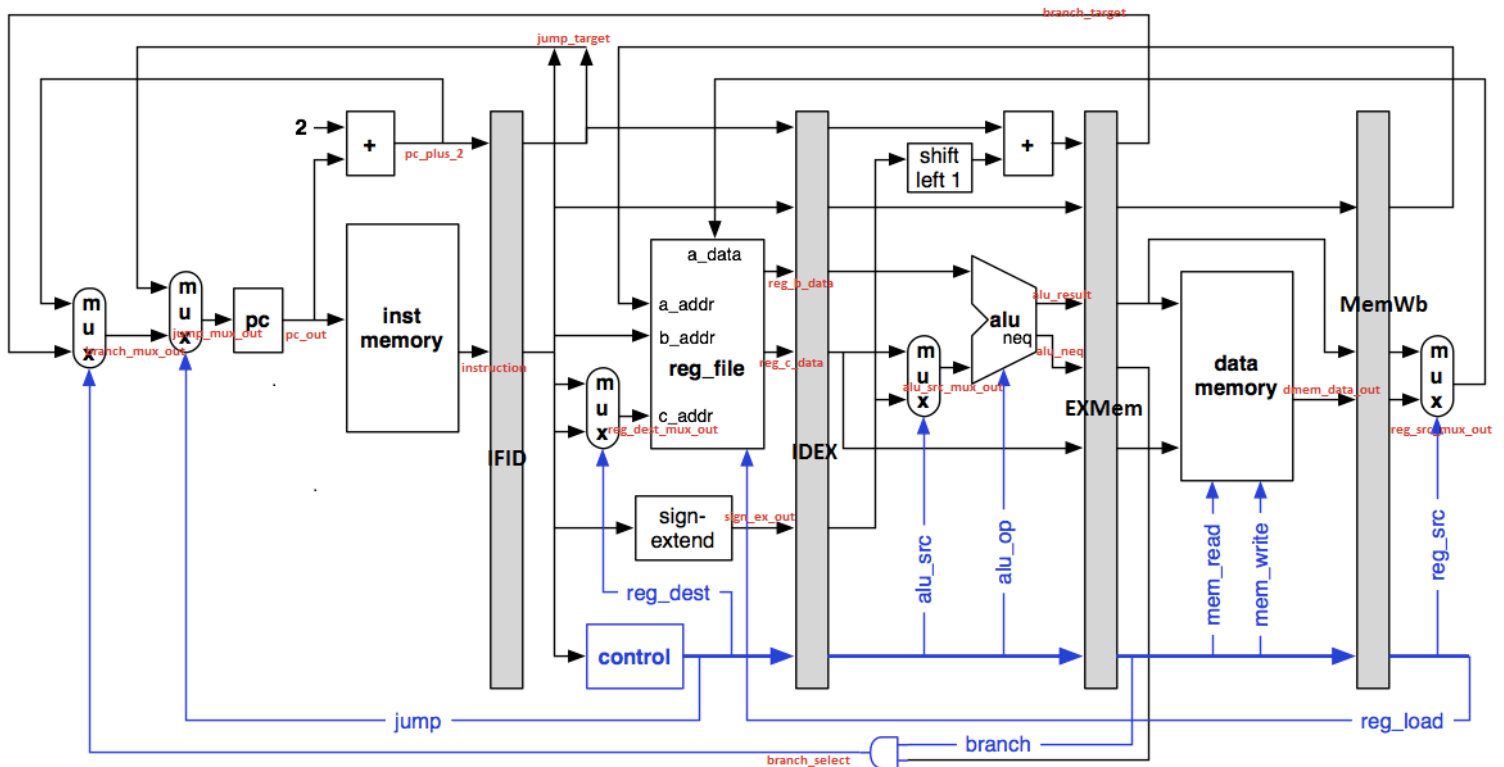

Since we are given the buffer VHDL code, the only implementation we need to do is in the system entity as well as changing the instruction_in memory file to accommodate for hazards. The main work was checking the diagram, going through and figuring out which signals I needed to replace with a buffer output signal. With these buffer output signals, the way they're constructed is by concatenating multiple signals together. For example, the first buffer has an input of $d \leq PC_count_plus_2 \& instruction$. So, in order to keep track of the signals, I

constructed a table that accurately keeps track of which signal goes where within the buffer so it was easier to connect everything in the system entity. I have attached this table to the end of the report with the instruction_in file. Other than that, the implementation was as simple as going through and changing any signals, for example anywhere I had an “instruction” signal as an input, it needed to be changed to IFID_out(15 downto 0) or whatever bits are necessary. After going through the whole datapath doing this and adding the necessary nops to avoid hazards, that was all that was needed to be done to complete the pipelined datapath.

Experimentation

The difficulty in this lab was not the concepts or the theory involved in the implementation, it was the confusion that could come up very easily because of all these loose signals. Building a table for all the signals was essential in getting this lab correct; without that to keep track of which signal was where, this lab would have been very difficult to complete. For a long time I was trying to run the simulation with the same instruction set we had in Lab 6, which was obviously going to give me some errors as it had not accounted for hazards.

Once I started going through the instruction_in file and changed up the instructions is where I began to actually see the success of the implementation. I went through the code and found where we had RAW data dependancies and added 3 nops. Along with that, I also needed to add some nops after any branch instructions. Once I was here, I still could not figure out why my code was not working, however the final step had not been completed. To finally get everything working, I also had to go through and recount the instructions and change where the branch and jump instructions are pointing to, since adding the nops changed up the instruction addressing a

Results

[illegible]

Conclusion

In conclusion, the pipelined datapath works as intended and we are now able to execute

instructions with a little more optimization. This lab was great at teaching how to modify an existing project as well as what goes into a pipelined datapath. I didn't think I'd have to spend as much time messing with the instruction_in file as I did, but turns out that was more than half the battle! Another useful piece of information I gained was how to do generic implementations, allowing the actual VHDL component creation to be made for many different uses.

Appdx

IF / ID (32 bits)

31 - 16 : PC + 2

15 - 0 : instruction

ID / EX (77 bits)

76 - 61 : PC + 2

60 - 57 : a_addr

56 - 41 : b_data

40 - 25 : c_data

24 - 9 : SE_output

8 : alusrc

7 - 5 : aluop

4 : branch

3 : readmem

2 : writemem

1 : regsrc

0 : regload

EX / MEM (58 bits)

57 - 42 : branch target

41 - 38 : a_addr

37 - 22 : alu_result

21 : alu_neq

20 - 5 : reg_c_data

4 : branch

3 : readmem

2 : writemem

1 : regsrc

0 : regload

MEM / WB (38 bits)

37 - 34 : a_addr

33 - 18 : alu_result

17 - 2 : data_mem_out

1 : regsrc

0 : regload

1	00000101
2	01000011
3	00000000
4	00000000
5	00000000
6	00000000
7	00000000
8	00000000
9	00000010
10	01000100
11	00000000
12	00000000
13	00000000
14	00000000
15	00000000
16	00000000
17	00000000
18	11000011
19	00000100
20	11000100
21	00000100
22	01000110
23	01100000
24	10000111
25	00000000
26	10001000
27	00000000
28	00000000
29	00000000
30	00000000
31	00000000
32	00000000
33	10000111
34	01110011
35	01111000
36	01111001
37	00000000
38	00000000
39	00000000
40	00000000
41	00000000
42	00000000
43	00010111
44	10011001
45	00000000
46	00000000
47	00000000
48	00000000
49	00000000
50	00000000
51	01110001
52	01000111
53	00010001
54	10110000
55	00000100
56	10001010
57	00000000
58	00000000
59	00001111
60	01001111